

FCC Exam Element 3 Question Pool for General Class  
Effective 7/1/2019 – 6/30/2023

**SUBELEMENT G5 – ELECTRICAL PRINCIPLES [3 Exam Questions – 3 Groups]**

G5A – Reactance; inductance; capacitance; impedance; impedance matching

G5A01

**What is impedance?**

- A. The electric charge stored by a capacitor
- B. The inverse of resistance
- C. The opposition to the flow of current in an AC circuit
- D. The force of repulsion between two similar electric fields

~~

G5A02

**What is reactance?**

- A. Opposition to the flow of direct current caused by resistance
- B. Opposition to the flow of alternating current caused by capacitance or inductance
- C. A property of ideal resistors in AC circuits
- D. A large spark produced at switch contacts when an inductor is de-energized

~~

G5A03

**Which of the following causes opposition to the flow of alternating current in an inductor?**

- A. Conductance
- B. Reluctance
- C. Admittance
- D. Reactance

~~

G5A04

**Which of the following causes opposition to the flow of alternating current in a capacitor?**

- A. Conductance
- B. Reluctance
- C. Reactance
- D. Admittance

~~

G5A05

**How does an inductor react to AC?**

- A. As the frequency of the applied AC increases, the reactance decreases
- B. As the amplitude of the applied AC increases, the reactance increases
- C. As the amplitude of the applied AC increases, the reactance decreases
- D. As the frequency of the applied AC increases, the reactance increases

~~

G5A06

**How does a capacitor react to AC?**

- A. As the frequency of the applied AC increases, the reactance decreases
- B. As the frequency of the applied AC increases, the reactance increases
- C. As the amplitude of the applied AC increases, the reactance increases
- D. As the amplitude of the applied AC increases, the reactance decreases

~~

G5A07

**What happens when the impedance of an electrical load is equal to the output impedance of a power source, assuming both impedances are resistive?**

- A. The source delivers minimum power to the load
- B. The electrical load is shorted
- C. No current can flow through the circuit
- D. The source can deliver maximum power to the load

~~

G5A08

**What is one reason to use an impedance matching transformer?**

- A. To minimize transmitter power output
- B. To maximize the transfer of power
- C. To reduce power supply ripple
- D. To minimize radiation resistance

~~

G5A09

**What unit is used to measure reactance?**

- A. Farad
- B. Ohm
- C. Ampere
- D. Siemens

~~

G5A10

**Which of the following devices can be used for impedance matching at radio frequencies?**

- A. A transformer
- B. A Pi-network
- C. A length of transmission line
- D. All these choices are correct

~~

G5A11

**Which of the following describes one method of impedance matching between two AC circuits?**

- A. Insert an LC network between the two circuits
- B. Reduce the power output of the first circuit
- C. Increase the power output of the first circuit
- D. Insert a circulator between the two circuits

~~

G5B – The decibel; current and voltage dividers; electrical power calculations; sine wave root-mean-square (RMS) values; PEP calculations

G5B01

**What dB change represents a factor of two increase or decrease in power?**

- A. Approximately 2 dB
- B. Approximately 3 dB
- C. Approximately 6 dB
- D. Approximately 12 dB

~~

G5B02

**How does the total current relate to the individual currents in each branch of a purely resistive parallel circuit?**

- A. It equals the average of each branch current
- B. It decreases as more parallel branches are added to the circuit
- C. It equals the sum of the currents through each branch
- D. It is the sum of the reciprocal of each individual voltage drop

~~

G5B03

**How many watts of electrical power are used if 400 VDC is supplied to an 800 ohm load?**

- A. 0.5 watts
- B. 200 watts
- C. 400 watts
- D. 3200 watts

~~

G5B04

**How many watts of electrical power are used by a 12 VDC light bulb that draws 0.2 amperes?**

- A. 2.4 watts
- B. 24 watts
- C. 6 watts
- D. 60 watts

~~

G5B05

**How many watts are dissipated when a current of 7.0 milliamperes flows through a 1250 ohm resistance?**

- A. Approximately 61 milliwatts
- B. Approximately 61 watts
- C. Approximately 11 milliwatts
- D. Approximately 11 watts

~~

G5B06

**What is the output PEP from a transmitter if an oscilloscope measures 200 volts peak-to-peak across a 50 ohm dummy load connected to the transmitter output?**

- A. 1.4 watts
- B. 100 watts
- C. 353.5 watts
- D. 400 watts

~~

G5B07

**What value of an AC signal produces the same power dissipation in a resistor as a DC voltage of the same value?**

- A. The peak-to-peak value
- B. The peak value
- C. The RMS value
- D. The reciprocal of the RMS value

~~

G5B08

**What is the peak-to-peak voltage of a sine wave with an RMS voltage of 120.0 volts?**

- A. 84.8 volts
- B. 169.7 volts
- C. 240.0 volts
- D. 339.4 volts

~~

G5B09

**What is the RMS voltage of a sine wave with a value of 17 volts peak?**

- A. 8.5 volts
- B. 12 volts
- C. 24 volts
- D. 34 volts

~~

G5B10

**What percentage of power loss would result from a transmission line loss of 1 dB?**

- A. 10.9 percent
- B. 12.2 percent
- C. 20.6 percent
- D. 25.9 percent

~~

G5B11

**What is the ratio of peak envelope power to average power for an unmodulated carrier?**

- A. 0.707
- B. 1.00
- C. 1.414
- D. 2.00

~~

G5B12

**What would be the RMS voltage across a 50 ohm dummy load dissipating 1200 watts?**

- A. 173 volts
- B. 245 volts
- C. 346 volts
- D. 692 volts

~~

G5B13

**What is the output PEP of an unmodulated carrier if an average reading wattmeter connected to the transmitter output indicates 1060 watts?**

- A. 530 watts
- B. 1060 watts
- C. 1500 watts
- D. 2120 watts

~~

G5B14

**What is the output PEP from a transmitter if an oscilloscope measures 500 volts peak-to-peak across a 50 ohm resistive load connected to the transmitter output?**

- A. 8.75 watts
- B. 625 watts**
- C. 2500 watts
- D. 5000 watts

~~

G5C – Resistors, capacitors, and inductors in series and parallel; transformers

G5C01

**What causes a voltage to appear across the secondary winding of a transformer when an AC voltage source is connected across its primary winding?**

- A. Capacitive coupling
- B. Displacement current coupling
- C. Mutual inductance**
- D. Mutual capacitance

~~

G5C02

**What happens if a signal is applied to the secondary winding of a 4:1 voltage step-down transformer instead of the primary winding?**

- A. The output voltage is multiplied by 4**
- B. The output voltage is divided by 4
- C. Additional resistance must be added in series with the primary to prevent overload
- D. Additional resistance must be added in parallel with the secondary to prevent overload

~~

G5C03

**Which of the following components increases the total resistance of a resistor?**

- A. A parallel resistor
- B. A series resistor**
- C. A series capacitor
- D. A parallel capacitor

~~

G5C04

**What is the total resistance of three 100 ohm resistors in parallel?**

- A. 0.30 ohms
- B. 0.33 ohms
- C. 33.3 ohms**
- D. 300 ohms

~~

G5C05

**If three equal value resistors in series produce 450 ohms, what is the value of each resistor?**

- A. 1500 ohms
- B. 90 ohms
- C. 150 ohms
- D. 175 ohms

~~

G5C06

**What is the RMS voltage across a 500-turn secondary winding in a transformer if the 2250-turn primary is connected to 120 VAC?**

- A. 2370 volts
- B. 540 volts
- C. 26.7 volts
- D. 5.9 volts

~~

G5C07

**What is the turns ratio of a transformer used to match an audio amplifier having 600 ohm output impedance to a speaker having 4 ohm impedance?**

- A. 12.2 to 1
- B. 24.4 to 1
- C. 150 to 1
- D. 300 to 1

~~

G5C08

**What is the equivalent capacitance of two 5.0 nanofarad capacitors and one 750 picofarad capacitor connected in parallel?**

- A. 576.9 nanofarads
- B. 1733 picofarads
- C. 3583 picofarads
- D. 10.750 nanofarads

~~

G5C09

**What is the capacitance of three 100 microfarad capacitors connected in series?**

- A. 0.30 microfarads
- B. 0.33 microfarads
- C. 33.3 microfarads
- D. 300 microfarads

~~

G5C10

**What is the inductance of three 10 millihenry inductors connected in parallel?**

- A. 0.30 henries
- B. 3.3 henries
- C. 3.3 millihenries
- D. 30 millihenries

~~

G5C11

**What is the inductance of a 20 millihenry inductor connected in series with a 50 millihenry inductor?**

- A. 0.07 millihenries
- B. 14.3 millihenries
- C. 70 millihenries
- D. 1000 millihenries

~~

G5C12

**What is the capacitance of a 20 microfarad capacitor connected in series with a 50 microfarad capacitor?**

- A. 0.07 microfarads
- B. 14.3 microfarads
- C. 70 microfarads
- D. 1000 microfarads

~~

G5C13

**Which of the following components should be added to a capacitor to increase the capacitance?**

- A. An inductor in series
- B. A resistor in series
- C. A capacitor in parallel
- D. A capacitor in series

~~

G5C14

**Which of the following components should be added to an inductor to increase the inductance?**

- A. A capacitor in series
- B. A resistor in parallel
- C. An inductor in parallel
- D. An inductor in series

~~

G5C15

**What is the total resistance of a 10 ohm, a 20 ohm, and a 50 ohm resistor connected in parallel?**

- A. 5.9 ohms
- B. 0.17 ohms
- C. 10000 ohms
- D. 80 ohms

~~

G5C16

**Why is the conductor of the primary winding of many voltage step-up transformers larger in diameter than the conductor of the secondary winding?**

- A. To improve the coupling between the primary and secondary
- B. To accommodate the higher current of the primary
- C. To prevent parasitic oscillations due to resistive losses in the primary
- D. To ensure that the volume of the primary winding is equal to the volume of the secondary winding

~~

G5C17

**What is the value in nanofarads (nF) of a 22,000 picofarad (pF) capacitor?**

- A. 0.22
- B. 2.2
- C. 22
- D. 220

~~

G5C18

**What is the value in microfarads of a 4700 nanofarad (nF) capacitor?**

- A. 47
- B. 0.47
- C. 47,000
- D. 4.7

~~